

CS-472 Design Technologies for Integrated Systems

Homework 2

David Desboeufs

October 23, 2022

1 Optimization

We want to optimize the following FIR filter:

$$y[n] = b_0x[n] + b_1x[n-1] + \dots + b_Nx[n-N]$$

First, to minimize the number of multiplications done, we can group each pair that share the same multiplication factor (i.e. b_0 and b_N , b_1 and b_{N-1} , \dots). This is possible due to the fact that constants are known.

$$y = 19(x_0 + x_9) + 390(x_1 + x_8) + 864(x_2 + x_7) + 3072(x_3 + x_6) + 9(x_4 + x_5)$$

Next step is to replace multiplications by additions, for example a multiplication by a factor 2 is a simple shift to the left by 1. Here we take 19 as example:

$$19 = 1 \ll 4 + 1 \ll 1 + 1$$

So to replace this multiplication we need to perform 2 shifts and 3 additions.

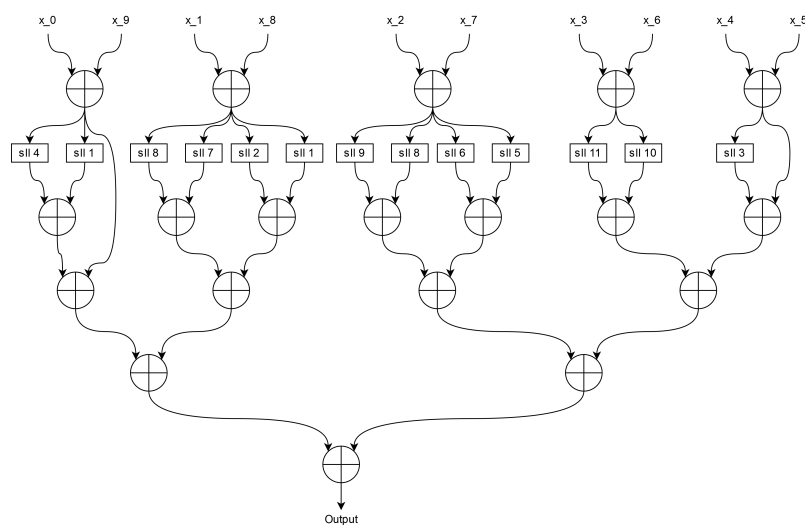


Figure 1: Data Flow

2 Results

```
clock global_clk (rise edge)          1.75    1.75
clock network delay (ideal)            0.00    1.75
R_o/Dout_reg[31]/CK (DFFRS_X1)        0.00    1.75 r
library setup time                     -0.03    1.72
data required time                      1.72
-----
data required time                      1.72
data arrival time                      -1.72
-----
slack (MET)                            0.00
```

Figure 2: Timing

```
Combinational area:                    546.083997
Buf/Inv area:                          87.846000
Noncombinational area:                 221.760006
Macro/Black Box area:                  0.000000
Net Interconnect area:                 540.448359

Total cell area:                       767.844003
Total area:                            1308.292362
```

Figure 3: Total Area

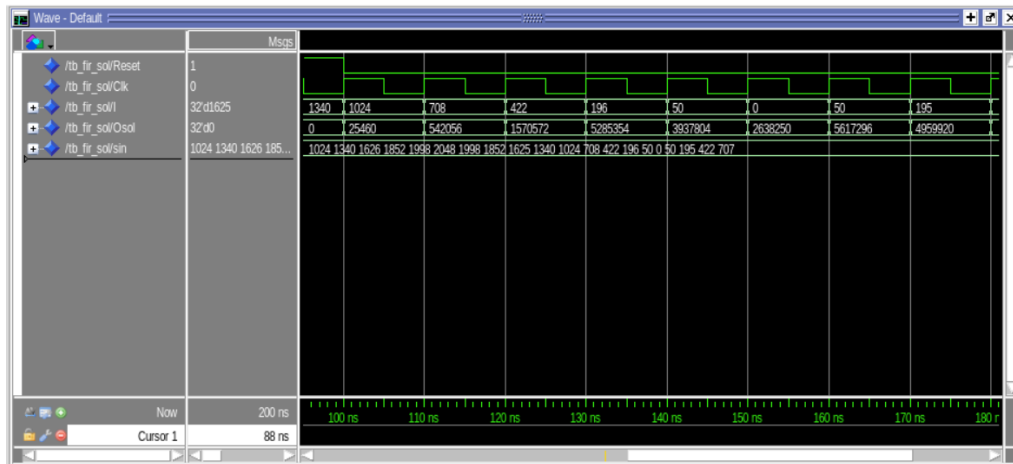


Figure 4: Modelsim Simulation